

گزارشکار آزمایش ۷

: RAM

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.math_real.all;

use ieee.Numeric_Std.all;

use ieee.std_logic_unsigned.all;

entity RAM is

generic (

    W :integer := 16; -- data width

    C :integer := 3 -- addr width

);

port (

    clk    :in  std_logic;           -- Clock Input

    address :in  std_logic_vector (C-1 downto 0);    -- address Input 3 bit

    data    :inout std_logic_vector (W-1 downto 0);    -- input or output data

    WR      :in  std_logic;           -- Write Enable

    RD      :in  std_logic;           -- Read Enable

    reset   :in  std_logic

);

end RAM;

architecture rt1 of RAM is

-- Internal variables

    signal data_out :std_logic_vector (W-1 downto 0);

    constant D :integer := 2**C; -- ram size

    type RAM is array (0 to D-1 )of std_logic_vector (W-1 downto 0);

    signal RAM_1: RAM := (others=>(others=>'0'));

begin

    data <= data_out when (reset ='1' and RD ='1') else(others =>'Z');

    process (reset,clk )
```

```

begin
  -- RESET_state:
  if(reset = '0' ) then
    -- some code --
  end if;

  -- RAM_1 Write Block
  -- Write Operation : When wr = 1, reset = 1
  if (rising_edge(clk)) then
    if (reset = '1' and WR = '1') then
      RAM_1(conv_integer(address)) <= data;
    end if;
  end if;

  -- RAM_1 Read Block
  -- Read Operation : When rd = 1, reset = 1
  if (rising_edge(clk)) then
    if (reset = '1' and RD = '1') then
      data_out <= RAM_1(conv_integer(address));
    end if;
  end if;

  end process;
end rt1;

```

: RAM_tb

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY RAM_tb IS

END RAM_tb;

ARCHITECTURE test OF RAM_tb IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT RAM

PORT(

clk : IN std_logic;

address : IN std_logic_vector(2 downto 0);

data : inout std_logic_vector (15 downto 0);

WR : IN std_logic;

RD : IN std_logic;

reset : IN std_logic

);

END COMPONENT;

--Inputs

signal clk : std_logic;

signal address : std_logic_vector(2 downto 0);

signal WR : std_logic ;

signal RD : std_logic ;

signal reset : std_logic ;

signal data : std_logic_vector(15 downto 0);

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: RAM PORT MAP (

clk => clk,

address => address,

data=> data,

WR => WR,

RD => RD,

reset => reset

);


clk <='0','1' after 150 ns , '0' after 300 ns , '1' after 450 ns , '0' after 600 ns, '1' after 750 ns;

```

address <= "000" , "001" after 450 ns , "000" after 750 ns;
data <= "0000000000000000" , "0000000000000001" after 450 ns;
WR <= '1' , '0' after 750 ns;
RD <= '0' , '1' after 750 ns;
reset <= '1';
END;

```

خروجی شبیه سازی RAM_tb :

 

: RAM_DUAL

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.math_real.all;

use ieee.Numeric_Std.all;

use ieee.std_logic_unsigned.all;

entity RAM_DUAL is
    generic (
        W :integer := 16; -- data width
        C :integer := 3 -- addr width
    );
    port (
        clk    :in  std_logic;           -- Clock Input
        address :in  std_logic_vector (C-1 downto 0); -- address Input 3 bit
        datai   :in  std_logic_vector (W-1 downto 0); -- input data
        WR      :in  std_logic;           -- Write Enable
        RD      :in  std_logic;           -- Read Enable
        reset   :in  std_logic;
        datao   :out std_logic_vector (W-1 downto 0) -- output data
    );
end RAM_DUAL;

architecture rt1 of RAM_DUAL is
    -- Internal variables
    signal data_out :std_logic_vector (W-1 downto 0);
    constant D :integer := 2**C; -- ram size
    type RAM_DUAL is array (0 to D-1 )of std_logic_vector (W-1 downto 0);
    signal RAM_DUAL_1: RAM_DUAL := (others=>(others=>'0'));
begin
    datao <= data_out when (reset = '1' and RD = '1') else(others =>'X');
```

```

    process (reset,clk )
    begin
        -- RESET_state:
        if(reset = '0') then
            ----- some code -----
        end if;

        -- RAM_1 Write Block
        -- Write Operation : When wr = 1, reset = 1
        if (rising_edge(clk)) then
            if (reset = '1' and WR = '1') then
                RAM_DUAL_1(conv_integer(address)) <= datai;
            end if;
        end if;

        -- RAM_1 Read Block
        -- Read Operation : When rd = 1, reset = 1
        if (rising_edge(clk)) then
            if (reset = '1' and RD = '1') then
                data_out <= RAM_DUAL_1(conv_integer(address));
            end if;
        end if;
    end process;
end rt1;

```

: RAM_DUAL_tb

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY RAM_DUAL_tb IS

END RAM_DUAL_tb;

```

ARCHITECTURE test OF RAM_DUAL_tb IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT RAM_DUAL

PORT(

clk : IN std_logic;

address : IN std_logic_vector(2 downto 0);

datai : IN std_logic_vector(15 downto 0);

WR : IN std_logic;

RD : IN std_logic;

reset : IN std_logic;

datao : OUT std_logic_vector(15 downto 0)

);

END COMPONENT;

--Inputs

signal clk : std_logic ;

signal address : std_logic_vector(2 downto 0);

signal datai : std_logic_vector(15 downto 0);

signal WR : std_logic ;

signal RD : std_logic ;

signal reset : std_logic;

--Outputs

signal datao : std_logic_vector(15 downto 0);

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: RAM_DUAL PORT MAP (

clk => clk,

address => address,

datai => datai,

datao => datao,


```

WR => WR,

RD => RD,

reset => reset

);

clk <= '0','1' after 150 ns , '0' after 300 ns , '1' after 450 ns , '0' after 600 ns, '1' after 750 ns;

address <= "000" , "001" after 450 ns , "000" after 750 ns;

datai <= "0000000000000000" , "0000000000000001" after 450 ns;

WR <= '1' , '0' after 750 ns;

RD <= '0' , '1' after 750 ns;

reset <= '1';

END;

```

خروجی شبیه سازی RAM_DUAL_tb :



: ROM

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all;

entity ROM is
port ( clk : in std_logic ;
      address : in std_logic_vector( 2 downto 0 );
      data_out : out std_logic_vector( 15 downto 0 ) );
end entity ;

architecture arch of ROM is

    type ROM is array ( 0 to 7 ) of std_logic_vector( 15 downto 0 ) ;
    constant ROM_1 : ROM := (
        0 => "0000000000000000" ,
        1 => "0000000000000001" ,
        2 => "0000000000000010" ,
        3 => "0000000000000011" ,
        4 => "0000000000000100" ,
        5 => "0000000000000101" ,
        6 => "0000000000000110" ,
        7 => "0000000000000111" ) ;

    begin
        process(clk)
            begin
                if( clk'event and clk = '1' ) then
                    data_out <= ROM_1(conv_integer(address)) ;
                end if ;
            end process ;
        end architecture ;
```

: ROM_tb

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY ROM_tb IS

END ROM_tb;

ARCHITECTURE behavior OF ROM_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT ROM

    PORT(

        clk : IN std_logic;

        address : IN std_logic_vector(2 downto 0);

        data_out : OUT std_logic_vector(15 downto 0)

    );

    END COMPONENT;

    --Inputs

    signal clk : std_logic ;

    signal address : std_logic_vector(2 downto 0) := (others => '0');

    --Outputs

    signal data_out : std_logic_vector(15 downto 0);

    BEGIN

        -- Instantiate the Unit Under Test (UUT)

        uut: ROM PORT MAP (

            clk => clk,

            address => address,

            data_out => data_out

        );

        clk <= '0', '1' after 150 ns , '0' after 300 ns , '1' after 450 ns , '0' after 600 ns , '1' after 750 ns;

        address <= "000" , "100" after 450 ns , "111" after 750 ns;

    END;
```

خروجی شبیه سازی ROM_tb :

