

گزارشکار آزمایش ۵

## : mux\_2to1

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity mux_2to1 is
port (
S,I0,I1 : in std_logic;
Y : out std_logic
);
end mux_2to1;
architecture structure of mux_2to1 is
signal C0,C1 : std_logic;
begin
C0 <= not S and I0;
C1 <= S and I1;
Y <= C0 or C1;
end structure;
```

---

## : DFF

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity DFF is
port(
Clk : in std_logic;
reset : in std_logic;
D : in std_logic;
Q : out std_logic
);
end DFF;
```

```

architecture Behavioral of DFF is
begin
process(Clk, reset)
begin
if (reset = '0') then Q <= '0';
elsif (rising_edge(Clk)) then Q <= D;
end if;
end process;
end Behavioral;

```

---

: PISO\_3bits

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity PISO_3bits is
port(
A: in std_logic_vector(2 downto 0);
S,Clk,reset : in std_logic;
B : out std_logic
);
end PISO_3bits;
architecture structure of PISO_3bits is
component mux_2to1 is
port (
S,I0,I1 : in std_logic;
Y : out std_logic
);
end component mux_2to1;
component DFF is
port(

```

```

    Clk : in std_logic;
    reset : in std_logic;
    D : in std_logic;
    Q : out std_logic
);
end component DFF;

signal s0,s1,s2,s3,s4 : std_logic;
begin
    mux_2 : mux_2to1 port map (S =>S , I0 => A(2),I1 => '0' , Y => s0);
    DFF_2 : DFF port map (Clk => Clk , reset => reset , D => s0 , Q =>s1);
    mux_1 : mux_2to1 port map (S =>S , I0 => A(1),I1 => s1 , Y => s2);
    DFF_1 : DFF port map (Clk => Clk , reset => reset , D => s2 , Q =>s3);
    mux_0 : mux_2to1 port map (S =>S , I0 => A(0),I1 => s3 , Y => s4);
    DFF_0 : DFF port map (Clk => Clk , reset => reset , D => s4 , Q =>B);
end structure;

```

---

### : PISO\_3bits\_tb

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY PISO_3bits_tb IS
END PISO_3bits_tb;
ARCHITECTURE test OF PISO_3bits_tb IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT PISO_3bits
        PORT(
            A : IN std_logic_vector(2 downto 0);
            S : IN std_logic;
            Clk : IN std_logic;
            reset : IN std_logic;

```

```

    B : OUT std_logic
);
END COMPONENT;

--Inputs
signal A : std_logic_vector(2 downto 0);
signal S : std_logic ;
signal Clk : std_logic ;
signal reset : std_logic ;


--Outputs
signal B : std_logic;

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: PISO_3bits PORT MAP (
        A => A,
        S => S,
        Clk => Clk,
        reset => reset,
        B => B
    );
    A <= "101";
    S <= '0' , '1' after 200 ns;
    clk <= '0' , '1' after 100 ns , '0' after 200 ns , '1' after 300 ns , '0' after 400 ns , '1' after 500 ns;
    reset <= '0' , '1' after 100 ns;
END;

```

---

## خروجی شبیه سازی : PIOS\_3bits\_tb

 

شمای مدار طراحی شده :

