

گزارش کار آزمایش ۳

D فلیپ فلاپ :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity DFF is
port(
    Clk : in std_logic;
    reset : in std_logic;
    D : in std_logic;
    Q : out std_logic
    );
end DFF;

architecture Behavioral of DFF is
begin
    process(Clk, reset)
    begin
        if (reset = '0') then Q <= '0';
        elsif (rising_edge(Clk)) then Q <= D;
        end if;
    end process;
end Behavioral;
```

: DFF_tb

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY DFF_tb IS
END DFF_tb;

ARCHITECTURE test OF DFF_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT DFF
```

```
PORT(
```

```
    Clk : IN std_logic;
```

```
    reset : IN std_logic;
```

```
    D : IN std_logic;
```

```
    Q : OUT std_logic
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal Clk : std_logic;
```

```
signal reset : std_logic;
```

```
signal D : std_logic;
```

```
--Outputs
```

```
signal Q : std_logic;
```

```
BEGIN
```

```
    -- Instantiate the Unit Under Test (UUT)
```

```
    uut: DFF PORT MAP (
```

```
        Clk => Clk,
```

```
        reset => reset,
```

```
        D => D,
```

```
        Q => Q
```

```

);

Clk <= '0' , '1' after 100 ns , '0' after 200 ns, '1' after 300 ns;


reset <= '0' , '1' after 100 ns , '0' after 300 ns ;

D <= '0' , '1' after 100 ns , '0' after 200 ns , '1' after 300 ns;

END;

```

خروجی شبیه سازی DFF_tb :

 

T فلیپ فلاپ :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TFF is
port ( T,reset,CLK : in std_logic;
      Q : out std_logic );
end TFF;

architecture Behavioral of TFF is
begin
    process(Clk,reset)
    variable temp: std_logic;
    begin
        if (reset = '0') then temp := '0';
        elsif (rising_edge(Clk)) then
            if T = '1' then temp := not temp;
            end if;
        end if;

        Q <= temp;
    end process;
end Behavioral;
```

: TFF_tb

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY TFF_tb IS
END TFF_tb;

ARCHITECTURE test OF TFF_tb IS
```

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT TFF

PORT(

 T : IN std_logic;

 reset : IN std_logic;

 CLK : IN std_logic;

 Q : OUT std_logic

);

END COMPONENT;

--Inputs

signal T : std_logic;

signal reset : std_logic;

signal CLK : std_logic;

--Outputs

signal Q : std_logic;

BEGIN

 -- Instantiate the Unit Under Test (UUT)

 uut: TFF PORT MAP (

 T => T,

 reset => reset,

 CLK => CLK,

 Q => Q

);


 T<='1','0' after 300 ns ;

 Clk <= '0' , '1' after 100 ns , '0' after 200 ns, '1' after 300 ns;

 reset <= '0', '1' after 100 ns;

END;

خروجی شبیه سازی TFF_tb :

 

: RippleCounter4bits

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RippleCounter4bits is
    Port ( CLK : in std_logic;
          reset : in std_logic;
          count : out std_logic_vector (3 downto 0)
        );
end RippleCounter4bits;
```

architecture Behavioral of RippleCounter4bits is

```
    component TFF
        port ( T,reset,CLK : in std_logic;
              Q : out std_logic );
    end component;

    signal s : std_logic_vector (3 downto 0);

begin
    T0: TFF port map(T=>'1', CLK=>CLK, reset => reset, Q=>s(0));
    T1: TFF port map(T=>'1', CLK=>not s(0), reset => reset,Q=>s(1));
    T2: TFF port map(T=>'1', CLK=>not s(1), reset => reset, Q=>s(2));
    T3: TFF port map(T=>'1', CLK=>not s(2), reset => reset, Q=>s(3));

    count <= s;
end Behavioral;
```

: RippleCounter4bits_tb

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY RippleCounter4bits_tb IS
END RippleCounter4bits_tb;
```


ARCHITECTURE test OF RippleCounter4bits_tb IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT RippleCounter4bits

PORT(

CLK : IN std_logic;

reset : IN std_logic;

count : OUT std_logic_vector(3 downto 0)

);

END COMPONENT;

--Inputs

signal CLK : std_logic;

signal reset : std_logic;

--Outputs

signal count : std_logic_vector(3 downto 0);

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: RippleCounter4bits PORT MAP (

CLK => CLK,

reset => reset,

count => count

);

```

-- Clock process definitions

Clk_process :process

begin

    Clk <= '0';

    wait for 32 ns;

    Clk <= '1';

    wait for 32 ns;


end process;

reset <= '0' , '1' after 32 ns;

END;

```

خروجی شبیه سازی : RippleCounter4bits_tb

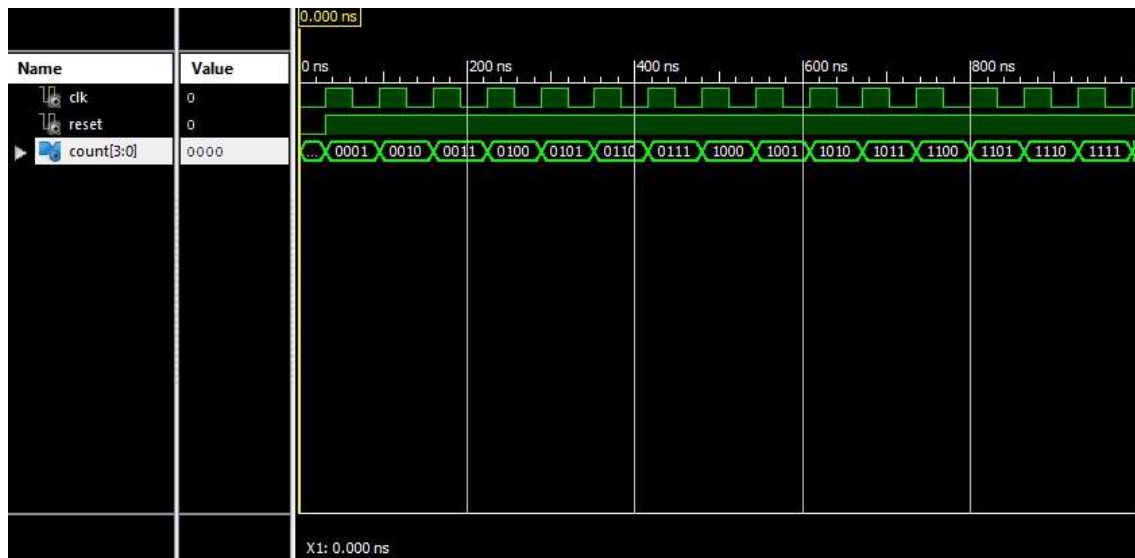

مدار Sequence detector برای رشته "۱۱۰۱" به صورت mealy :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mealy is
    Port ( clk : in STD_LOGIC;
          din : in STD_LOGIC;
          rst : in STD_LOGIC;
          dout : out STD_LOGIC
        );
end mealy;

architecture Behavioral of mealy is
    type state is (st0, st1, st2, st3);
    signal present_state, next_state : state;
begin
    synchronous_process: process (clk)
    begin
        if rising_edge(clk) then
            if (rst = '1') then
                present_state <= st0;
            else
                present_state <= next_state;
            end if;
        end if;
    end process;

    output_decoder : process(present_state, din)
    begin
        next_state <= st0;
        case (present_state) is
```

```
when st0 =>
  if (din = '1') then
    next_state <= st1;
    dout <= '0';
  else
    next_state <= st0;
    dout <= '0';
  end if;
when st1 =>
  if (din = '1') then
    next_state <= st2;
    dout <= '0';
  else
    next_state <= st0;
    dout <= '0';
  end if;
when st2 =>
  if (din = '0') then
    next_state <= st3;
    dout <= '0';
  else
    next_state <= st2;
    dout <= '0';
  end if;
when st3 =>
  if (din = '1') then
    next_state <= st1;
    dout <= '1';
  else
```

```

        next_state <= st0;
        dout <= '0';
    end if;
    when others =>
        next_state <= st0;
    end case;
end process;
end Behavioral;

```

مدار Sequence detector برای رشته "۱۱۰۱" به صورت moore :

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity moore is
    Port ( clk : in STD_LOGIC;
          din : in STD_LOGIC;
          rst : in STD_LOGIC;
          dout : out STD_LOGIC
        );
end moore;

architecture Behavioral of moore is
    type state is (st0, st1, st2, st3, st4);
    signal present_state, next_state : state;
    begin
        synchronous_process: process (clk)
        begin
            if rising_edge(clk) then
                if (rst = '1') then
                    present_state <= st0;
                else

```

```
        present_state <= next_state;
    end if;
end if;
end process;
next_state_decoder : process(present_state, din)
begin
    next_state <= st0;
    case (present_state) is
        when st0 =>
            if (din = '1') then
                next_state <= st1;
            else
                next_state <= st0;
            end if;
        when st1 =>
            if (din = '1') then
                next_state <= st2;
            else
                next_state <= st0;
            end if;
        when st2 =>
            if (din = '0') then
                next_state <= st3;
            else
                next_state <= st2;
            end if;
        when st3 =>
            if (din = '1') then
                next_state <= st4;
```

```

        else
            next_state <= st0;
        end if;
    when st4 =>
        if (din = '1') then
            next_state <= st2;
        else
            next_state <= st0;
        end if;
    when others =>
        next_state <= st0;
    end case;
end process;
output_decoder : process(present_state)
begin
    case (present_state) is
        when st0 =>
            dout <= '0';
        when st1 =>
            dout <= '0';
        when st2 =>
            dout <= '0';
        when st3 =>
            dout <= '0';
        when st4 =>
            dout <= '1';
        when others =>
            dout <= '0';
    end case;

```

```
end process;  
end Behavioral;
```

مدار moore و mealy بالا به صورت مجتمع :

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
entity moore_mealy is  
    port(  
        din : in std_logic ;  
        dout_moore ,dout_mealy : out std_logic;  
        Clk : in std_logic;  
        Rst : in std_logic  
    );  
end moore_mealy;  
architecture Behavioral of moore_mealy is  
    component mealy is  
        port(  
            din : in std_logic ;  
            dout : out std_logic;  
            clk : in std_logic;  
            rst : in std_logic  
        );  
    end component mealy;  
    component moore is  
        port(  
            din : in std_logic ;  
            dout : out std_logic;  
            clk : in std_logic;
```



```

        rst : in std_logic
    );

end component moore;

begin

    mealy_state_machine: mealy port map(din => din , dout => dout_mealy,clk => Clk ,
rst => Rst);

    moore_state_machine: moore port map(din => din , dout => dout_moore , clk => Clk
, rst => Rst);

end Behavioral;

```

: Moore_mealy_tb

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY moore_mealy_tb IS

END moore_mealy_tb;

ARCHITECTURE test OF moore_mealy_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT moore_mealy

    PORT(

        din : IN  std_logic;

        dout_moore : OUT  std_logic;

        dout_mealy : OUT  std_logic;

        Clk : IN  std_logic;

        Rst : IN  std_logic

    );

    END COMPONENT;

    --Inputs

    signal din : std_logic := '0';

    signal Clk : std_logic ;

```

```

signal Rst : std_logic ;

--Outputs

signal dout_moore : std_logic;
signal dout_mealy : std_logic;

-- Clock period definitions
constant Clk_period : time := 80 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)

    uut: moore_mealy PORT MAP (
        din => din,
        dout_moore => dout_moore,
        dout_mealy => dout_mealy,
        Clk => Clk,
        Rst => Rst
    );

    -- Clock process definitions
    Clk_process :process
    begin

        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;

    end process;

    -- Stimulus process
    stim_proc: process
    begin
        Rst <= '1' ;
        wait for 3*Clk_period/2;
        Rst <= '0' ;
    end process;


```

```

din <= '1' ;
wait for Clk_period;
din <= '1' ;
wait for Clk_period;
din <= '0' ;
wait for Clk_period;
din <= '1' ;
wait for Clk_period;
din <= '0' ;
wait;
end process;
END;

```

خروجی شبیه سازی moore_mealy_tb :

 

مدار تشخیص دورشته "۰۱۱۰" و "۰۱۰۱" به صورت moore :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity moore_0101_or_0110 is
    Port ( clk : in STD_LOGIC;
          din : in STD_LOGIC;
          rst : in STD_LOGIC;
          p_state : out std_logic_vector(2 downto 0);
          n_state : out std_logic_vector(2 downto 0);
          dout : out STD_LOGIC);
end moore_0101_or_0110;

architecture Behavioral of moore_0101_or_0110 is
    type state is (st0, st1, st2, st3, st4, st5, st6);
    signal present_state, next_state : state;
    begin
        synchronous_process: process (clk)
        begin
            if rising_edge(clk) then
                if (rst = '1') then
                    present_state <= st0;
                else
                    present_state <= next_state;
                end if;
            end if;
        end process;

        next_state_decoder : process(present_state,din)
        begin
            case (present_state) is
                when st0 =>
```

```
    if (din = '0') then
        next_state <= st1;
        n_state <= "001";
    else
        next_state <= st0;
        n_state <= "000";
    end if;
when st1 =>
    if (din = '1') then
        next_state <= st2;
        n_state <= "010";
    else
        next_state <= st1;
        n_state <= "001";
    end if;
when st2 =>
    if (din = '1') then
        next_state <= st4;
        n_state <= "100";
    else
        next_state <= st3;
        n_state <= "011";
    end if;
when st3 =>
    if (din = '1') then
        next_state <= st6;
        n_state <= "110";
    else
        next_state <= st1;
        n_state <= "001";
```

```
        end if;
    when st4 =>
        if (din = '1') then
            next_state <= st0;
            n_state <= "000";
        else
            next_state <= st5;
            n_state <= "101";
        end if;
    when st5 =>
        if (din = '1') then
            next_state <= st2;
            n_state <= "010";
        else
            next_state <= st1;
            n_state <= "001";
        end if;
    when st6 =>
        if (din = '1') then
            next_state <= st4;
            n_state <= "100";
        else
            next_state <= st3;
            n_state <= "011";
        end if;
    when others =>
        next_state <= st0;
        n_state <= "000";
end case;
```

```
end process;

output_decoder : process(present_state)
begin
    case (present_state) is
        when st0 =>
            dout <= '0';
            p_state <= "000";
        when st1 =>
            dout <= '0';
            p_state <="001";
        when st2 =>
            dout <= '0';
            p_state <= "010";
        when st3 =>
            dout <= '0';
            p_state <= "011";
        when st4 =>
            dout <= '0';
            p_state <= "100";
        when st5 =>
            dout <= '1';
            p_state <= "101";
        when st6 =>
            dout <= '1';
            p_state <= "110";
        when others =>
            dout <= '0';
            p_state <= "111";
    end case;
end;
```

```
        end case;
    end process;
end Behavioral;
```

: moore_0101_or_0110_tb

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY moore_0101_or_0110_tb IS
END moore_0101_or_0110_tb;
ARCHITECTURE test OF moore_0101_or_0110_tb IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT moore_0101_or_0110
    PORT(
        clk : IN  std_logic;
        din : IN  std_logic;
        rst : IN  std_logic;
        p_state : out std_logic_vector(2 downto 0);
        n_state : out std_logic_vector(2 downto 0);
        dout : OUT std_logic
    );
    END COMPONENT;
    --Inputs
    signal clk : std_logic ;
    signal din : std_logic := '1';
    signal rst : std_logic ;
    --Outputs
    signal dout : std_logic;
    signal p_state : std_logic_vector(2 downto 0);
```



```

signal n_state : std_logic_vector(2 downto 0);

-- Clock period definitions

constant clk_period : time := 80 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)

    uut: moore_0101_or_0110 PORT MAP (

        clk => clk,

        din => din,

        rst => rst,

        p_state => p_state,

        n_state => n_state,

        dout => dout

    );

    -- Clock process definitions

    clk_process : process

    begin

        clk <= '0';

        wait for clk_period/2;

        clk <= '1';

        wait for clk_period/2;

    end process;

    -- Stimulus process

    stim_proc: process

    begin

        Rst <= '1' ;

        wait for Clk_period;

        Rst <= '0' ;

        wait for Clk_period *3/2;

        din <= '0' ;

```

```

wait for Clk_period ;

din <= '1' ;

wait for Clk_period ;

din <= '1' ;

wait for Clk_period ;

din <= '0' ;

wait for Clk_period;

din <= '1' ;

wait for Clk_period ;

din <= '0' ;

wait for Clk_period ;

din <= '1' ;

wait for Clk_period ;

din <= '1' ;

wait;

end process;

END;

```

خروجی شبیه سازی moore_0101_or_0110_tb :

